



ΠΑΝΕΠΙΣΤΗΜΙΟ
ΔΥΤΙΚΗΣ ΑΤΤΙΚΗΣ
UNIVERSITY OF WEST ATTICA

DEPARTMENT OF INFORMATION AND COMPUTER ENGINEERING

SEMESTER EXERCISE 2023

SIMPLE CIRCLE MIPS PROCESSOR

STUDENT DETAILS

NAME: ATHANASIOU VASILEIOS EVANGELOS

STUDENT ID: 19390005

STUDENT SEMESTER: 8th

STUDENT STATUS: UNDERGRADUATE

STUDY PROGRAM: UNIWA

THEORY DEPARTMENT: DEPARTMENT 2 KARKAZIS PANAGIOTIS

THEORY RESPONSIBLE: VOGIATZIS IOANNIS – KARKAZIS PANAGIOTIS

DELIVERY DATE: 15/9/2023

DESIGN OF DIGITAL SYSTEMS

STUDENT PHOTO:



DESIGN OF DIGITAL SYSTEMS

CONTENTS

1. Description of the circuit (PAGES 4-6)
2. Circuit code and testbench (PAGES 7-53)
3. Screenshot from the execution (PAGES 54-56)

DESIGN OF DIGITAL SYSTEMS

3. Data Memory

The data memory contains a memory address and the data stored in a Register read register File . Also, there are 2 read and write control signals connected to the Control Unit, MemRead and MemWrite , respectively. The data memory output is used to write to the Register File , as long as the appropriate control signals have been activated by the Control Unit.

4. Memory of Commands

The instruction memory contains a memory address for input and the instruction corresponding to that address for output.

5. Control Unit

The control unit contains appropriate control signals to determine the corresponding functions that other processor components are attempting to perform.

ALU Control Unit

Every command that belongs to a certain category, e.g. type R (add , addi ...) has a bit as well opcode , which is the main control signal for the ALU to know which instruction to execute.

7. PC

The program counter contains the address of the next instruction to be executed and is essentially a simple 32-bit register .

8. 5-fold 2-in-1 multiplexer

The multiplexer is a sequential circuit that, depending on the control signal, transmits the corresponding input to the output. Depending on the control signal RegDst of the Control Unit, the multiplexer transfers the corresponding 5- bit information from the command entered from the command memory, to the register of the Register File .

16-by-32 character extension unit

The sign extension unit converts the 16- bit number to 32- bit in order to add to the 32- bit adder .

10 . 32-way 2-in-1 multiplexer

This multiplexer transmits accordingly the " ALUSrc " control bit of the control unit, the corresponding information to the input of the ALU .

1 1. 32-way multiplexer 2-in-1

DESIGN OF DIGITAL SYSTEMS

This multiplexer accordingly transmits the " MemtoReg " control bit of the control unit, the corresponding information in the data of the Register File .

12. 32-fold 2-in-1 multiplexer

This multiplexer forwards the Branch result accordingly AND Zero of the control unit and the ALU respectively, the corresponding information at the Program input Counter .

13. Shift Unit left by 2 (32- bits)

The shift unit shifts the information by 2- bits to the left, so that the overflow phenomenon does not occur in the addition.

14. Adder 32 bits

The adder adds the address contained in the program counter by 1 for the next command to be executed.

15. Adder 32 bits

The adder that adds the program address counter incremented by 1 with the information shifted 2 bits left.

2-input AND gate

AND gate which has as input the control signal Branch of the control unit and the output signal Zero of the ALU .

MIPS

The proper connection of the aforementioned components constitutes the single-cycle MIPS processor . Essentially, the operation of MIPS is described as follows:

1. Retrieve the address of the command from the program counter
2. Decoding the command from the command memory and transferring it to the registers of the Register File and at the entrance of the Control Unit
3. Carrying out the appropriate checks to transfer the information to the inputs of the ALU
4. Execution of the command
5. storage in memory
6. Calculation of the address of the next instruction to be executed.

DESIGN OF DIGITAL SYSTEMS

2. Circuit code and testbench

1. ALU

alu.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all ;
USE ieee.std_logic_signed.all ;

ENTITY alu IS
PORT (
    operationSig : IN std_logic_vector (3 DOWNTO 0);
    ALU_input1 : IN std_logic_vector (31 DOWNTO 0);
    ALU_input2 : IN std_logic_vector (31 DOWNTO 0);
    ALU_output : OUT std_logic_vector (31 DOWNTO 0);
    zeroSig : OUT std_logic );
END alu ;

ARCHITECTURE behavioral OF alu IS
BEGIN
    PROCESS( operationSig )
    VARIABLE tempInt : integer := 0;
    BEGIN
    CASE operationSig IS
    WHEN "0001" => -- add
        zeroSig <= '0 ';
        tempInt := to_integer (signed(ALU_input1) +
signed(ALU_input2));
        ALU_output <= std_logic_vector ( to_signed ( tempInt , 32 ));
    WHEN "0100" => -- add
        zeroSig <= '0 ';
        tempInt := to_integer (signed(ALU_input1) +
signed(ALU_input2));
```

DESIGN OF DIGITAL SYSTEMS

```
        ALU_output <= std_logic_vector ( to_signed ( tempInt , 32 ));
WHEN "0101" => -- sub
        tempInt := to_integer (signed(ALU_input1) -
signed(ALU_input2));
IF tempInt = 0 THEN
        zeroSig <= '1 ';
ELSE
        zeroSig <= '0 ';
END IF?

        ALU_output <= std_logic_vector ( to_signed ( tempInt , 32 ));
WHEN "1000" => -- bne
        tempInt := to_integer (signed(ALU_input1) -
signed(ALU_input2));
IF tempInt = 0 THEN
        zeroSig <= '1 ';
ELSE
        zeroSig <= '0 ';
END IF?

        ALU_output <= ALU_input1 XOR ALU_input2 ;
WHEN others =>
        zeroSig <= '0 ';
        ALU_output <= (others => '0' );
END CASE?
END PROCESS?
END behavioral?
```

alu_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY alu_tb IS
END alu_tb ;

ARCHITECTURE testbench OF alu_tb IS
```


DESIGN OF DIGITAL SYSTEMS

```
COMPONENT alu
PORT (
    operationSig : IN std_logic_vector (3 DOWNT0 0);
    ALU_input1 : IN std_logic_vector (31 DOWNT0 0);
    ALU_input2 : IN std_logic_vector (31 DOWNT0 0);
    ALU_output : OUT std_logic_vector (31 DOWNT0 0);
    zeroSig : OUT std_logic );
END COMPONENT;

SIGNAL operationSig_tb : std_logic_vector (3 DOWNT0 0);
, ALU_input2_tb, ALU_output_tb : std_logic_vector (31 DOWNT0 0);
SIGNAL zeroSig_tb : std_logic ;

BEGIN
    Comp_Connection : alu PORT MAP ( operationSig => operationSig_tb,
    ALU_input 1 = > ALU_input1_tb,
    ALU_input 2 = > ALU_input2_tb,
    zeroSig => zeroSig_tb,
    ALU_output => ALU_output_tb );

PROCESS
BEGIN
-- add
    operationSig_tb <= "0001 ";
    ALU_input1_tb <= "000000000000000000000000000001111 ";
    ALU_input2_tb <= "000000000000000000000000000000001 ";
    wait for 10 ns;

-- add
    operationSig_tb <= "0100 ";
    ALU_input1_tb <= "000000000000000000000000000001111 ";
    ALU_input2_tb <= "000000000000000000000000000000001 ";
```

DESIGN OF DIGITAL SYSTEMS

```
wait for 10 ns?

-- sub (zero)
    operationSig_tb <= "0101 ";
ALU_input1_tb <= "00000000000000000000000000001111 ";
ALU_input2_tb <= "00000000000000000000000000001111 ";
wait for 10 ns?

-- sub ( non zero )
    operationSig_tb <= "0101 ";
ALU_input1_tb <= "00000000000000000000000000001111 ";
ALU_input2_tb <= "00000000000000000000000000000001 ";
wait for 10 ns?

-- bne (equal)
    operationSig_tb <= "1000 ";
ALU_input1_tb <= "00000000000000000000000000001111 ";
ALU_input2_tb <= "00000000000000000000000000001111 ";
wait for 10 ns?

-- bne (not equal)
    operationSig_tb <= "1000 ";
ALU_input1_tb <= "00000000000000000000000000001111 ";
ALU_input2_tb <= "00000000000000000000000000000001 ";
wait for 10 ns?

END PROCESS?
END testbench?
```

2. Register File

register_file.vhd

```
LIBRARY ieee ;
```

DESIGN OF DIGITAL SYSTEMS

```
USE ieee.std_logic_1164.all;

USE ieee.std_logic_unsigned.all ;

USE ieee.numeric_std.ALL ;


ENTITY register_file IS
PORT (

        RF_clock      : IN std_logic ;
        RF_reset      : IN std_logic ;

readReg1 : IN std_logic_vector (4 DOWNT0 0);
readReg2 : IN std_logic_vector (4 DOWNT0 0);
        writeRegIn   : IN std_logic_vector (4 DOWNT0 0);
        writeData    : IN std_logic_vector (31 DOWNT0 0);
        RegWrite     : IN std_logic ;

readData1 : OUT std_logic_vector (31 DOWNT0 0);
readData2 : OUT std_logic_vector (31 DOWNT0 0));
END register_file ;


ARCHITECTURE behavioral OF register_file IS
TYPE regArray IS ARRAY( 0 TO 15) OF std_logic_vector (31 DOWNT0 0);
SIGNAL register_file : regArray ;


BEGIN

    PROCESS( RF_clock , RegWrite , RF_reset )
    BEGIN
        IF rising_ edge ( RF_clock ) THEN
            IF RegWrite = '1' THEN
                register_file ( to_integer (unsigned( writeRegIn ))) <= writeData
                ;
            END IF?
        END IF?

        readData1 <= register_file ( to_integer (unsigned(readReg1)) );
        readData2 <= register_file ( to_integer (unsigned(readReg2)) );
        IF RF_reset = '1' THEN
            readData1 <= (others => '0' );
        
```

DESIGN OF DIGITAL SYSTEMS

```
readData2 <= (others => '0' );  
END IF?  
END PROCESS?  
END behavioral?
```

register_file_tb.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
  
ENTITY register_file_tb IS  
END register_file_tb ;  
  
ARCHITECTURE testbench OF register_file_tb IS  
  
    COMPONENT register_file  
    PORT (  
        RF_clock      : IN std_logic ;  
        RF_reset      : IN std_logic ;  
        readReg1 : IN std_logic_vector (4 DOWNTO 0);  
        readReg2 : IN std_logic_vector (4 DOWNTO 0);  
        writeRegIn  : IN std_logic_vector (4 DOWNTO 0);  
        writeData   : IN std_logic_vector (31 DOWNTO 0);  
        RegWrite    : IN std_logic ;  
        readData1  : OUT std_logic_vector (31 DOWNTO 0);  
        readData2  : OUT std_logic_vector (31 DOWNTO 0));  
    END COMPONENT;  
  
    SIGNAL readReg1_tb, readReg2_tb , writeRegIn_tb : std_logic_vector (4  
DOWNTO 0);  
  
    SIGNAL writeData_tb , readData1_tb, readData2_ tb : std_logic_vector (31  
DOWNTO 0);  
  
    SIGNAL RegWrite_tb , RF_clock_tb , RF_reset_tb : std_logic ;  
  
BEGIN
```

DESIGN OF DIGITAL SYSTEMS

```
Comp_Connection : register_file PORT MAP ( RF_clock => RF_clock_tb,
                                             RF_reset => RF_reset_tb,

readReg1 => readReg1_tb,
readReg2 => readReg2_tb,

writeRegIn =>
writeRegIn_tb,

writeData => writeData_tb,
RegWrite => RegWrite_tb,

readData1 => readData1_tb,
readData2 => readData2_tb );

clock_process : PROCESS
BEGIN

    RF_clock_tb <= '0 ';

wait for 5 ns?

    RF_clock_tb <= '1 ';

wait for 5 ns?
END PROCESS?

stim_process : PROCESS
BEGIN

-- Perform write operation

    RF_reset_tb <= '0 ';
    writeRegIn_tb <= "00001 ";
    writeData_tb <= "11110000111100001111000011110000 ";
    RegWrite_tb <= '1 ';

WAIT FOR 10 ns?

-- Perform read operation
readReg1_tb <= "00001 ";
readReg2_tb <= "00010 ";

    RegWrite_tb <= '0 ';

WAIT FOR 10 ns?
```

DESIGN OF DIGITAL SYSTEMS

```
-- Reset the register file

        RF_reset_tb <= '1 ' ;

WAIT FOR 10 ns?

        RF_reset_tb <= '0 ' ;

        WAIT?

-- End the simulation

        WAIT?

END PROCESS?

END testbench?
```

3. Memory Data

data_memory.vhd

```
LIBRARY ieee ;

USE ieee.std_logic_1164.all;

USE ieee.numeric_std.all ;

ENTITY data_memory IS

PORT (

        writeData  : IN std_logic_vector (31 DOWNT0 0);
        addr       : IN std_logic_vector (31 DOWNT0 0);
        MemRead    : IN std_logic ;
        MemWrite   : IN std_logic ;
        readData   : OUT std_logic_vector (31 DOWNT0 0));

END data_memory ;

ARCHITECTURE behavioral OF data_memory IS

TYPE regArray IS ARRAY( 0 TO 15) OF std_logic_vector (31 DOWNT0 0);

SIGNAL data_memory : regArray := (others => (others => '0'));

SIGNAL address : integer;

BEGIN
```

DESIGN OF DIGITAL SYSTEMS

```
address <= to_integer ( unsigned( writeData ) ) WHEN
( to_integer (unsigned( writeData ) ) >= 0) ELSE 0;
    data_memory (address) <= writeData WHEN MemWrite = '1 ';
    readData <= data_memory (address) WHEN MemRead = '1 ';

END behavioral?
```

data_memory_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY data_memory_tb IS
END data_memory_tb ;

ARCHITECTURE testbench OF data_memory_tb IS

COMPONENT data_memory
PORT (
    writeData : IN std_logic_vector (31 DOWNT0 0);
    addr       : IN std_logic_vector (31 DOWNT0 0);
    MemRead    : IN std_logic ;
    MemWrite   : IN std_logic ;
    readData   : OUT std_logic_vector (31 DOWNT0 0));
END COMPONENT;

SIGNAL MemRead_tb , MemWrite_tb : std_logic ;
SIGNAL writeData_tb , addr_tb , readData_tb : std_logic_vector (31 DOWNT0 0);

BEGIN

    Comp_Connection : data_memory PORT MAP ( writeData => writeData_tb,
                                              addr => addr_tb,
                                              MemRead => MemRead_tb,
```

DESIGN OF DIGITAL SYSTEMS

```
MemWrite => MemWrite_tb,
readData => readData_tb );

PROCESS
BEGIN

    writeData_tb <= (others => '0' );
    addr_tb <= (others => '0' );
    MemRead_tb <= '0 ';
    MemWrite_tb <= '0 ';
    wait for 10 ns?

    writeData_tb <= "11110000111100001111000011110000 ";
    addr_tb <= "00000000000000000000000000000001 ";
    MemWrite_tb <= '1 ';
    wait for 10 ns?

    addr_tb <= "00000000000000000000000000000001 ";
    MemRead_tb <= '1 ';
    wait for 10 ns?

    writeData_tb <= "00001111000011110000111100001111 ";
    addr_tb <= "00000000000000000000000000000010 ";
    MemWrite_tb <= '1 ';
    wait for 10 ns?

    addr_tb <= "00000000000000000000000000000010 ";
    MemRead_tb <= '1 ';
    wait for 10 ns?
END PROCESS?
END testbench?
```

4. Memory Commands

DESIGN OF DIGITAL SYSTEMS

instructions_memory.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all ;

ENTITY instructions_memory IS
PORT (
    readAddr  : IN std_logic_vector (31 DOWNTO 0);
    instrOut   : OUT std_logic_vector (31 DOWNTO 0));
END instructions_memory ;

ARCHITECTURE behavioral OF instructions_memory IS
TYPE regArray IS ARRAY( 0 TO 15) OF std_logic_vector (31 DOWNTO 0);
SIGNAL instructions_memory : regArray := (
    "00100000000000110000000000000001", -- addi $3, $0, 1
    "00100000000000101000000000000011", -- addi $3, $0, 1
    "00000000011000000011001000000000", -- L1: add $6, $3, $0
    "10101100100001100000000000000000", -- sw $6, 0($4)
    "00100000011000110000000000000001", -- addi $3, $3, 1
    "00100000100001000000000000000001", -- addi $4, $4, 1
    "00100000101001011111111111111111", -- addi $5, $5, -1
    "00010100101000001111111111101010", -- bne $ 5.$ 0.L1
    others => (others => '0')
);

SIGNAL instrAddr : integer;
SIGNAL instruction : std_logic_vector (31 DOWNTO 0);
BEGIN
    instrAddr <= to_integer (unsigned( readAddr )) WHEN ( to_integer
(unsigned( readAddr )) >= 0) ELSE 0;
    instruction <= instructions_memory ( instrAddr ) WHEN ( instrAddr >= 0 )
    ELSE std_logic_vector ( to_signed (-1, 32));
    instrOut <= instruction;
END behavioral;
```

DESIGN OF DIGITAL SYSTEMS

instructions_memory_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY instructions_memory_tb IS
END instructions_memory_tb ;

ARCHITECTURE testbench OF instructions_memory_tb IS

COMPONENT instructions_memory
PORT (
    readAddr    : IN std_logic_vector (31 DOWNTO 0);
    instrOut     : OUT std_logic_vector (31 DOWNTO 0));
END COMPONENT;

SIGNAL readAddr_tb , instrOut_ tb : std_logic_vector (31 DOWNTO 0);

BEGIN

    Comp_Connection : instructions_memory PORT MAP ( readAddr =>
readAddr_tb,

                                                    instrOut => instrOut_tb );

PROCESS
BEGIN
    readAddr_tb <= "00000000000000000000000000000001"; -- Read address 1
wait for 10 ns?

    readAddr_tb <= "00000000000000000000000000000010"; -- Read address 2
wait for 10 ns?

    readAddr_tb <= "00000000000000000000000000000011"; -- Read address 3
wait for 10 ns?
END PROCESS?
```

DESIGN OF DIGITAL SYSTEMS

END testbench?

5. Unit Control

control_unit.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY control_unit IS
PORT (
    CU_clock : IN std_logic ;
    Instr    : IN std_logic_vector (5 DOWNTO 0);
    RegDst   : OUT std_logic ;
    Branch   : OUT std_logic ;
    MemRead  : OUT std_logic ;
    MemtoReg : OUT std_logic ;
    ALUOp    : OUT std_logic_vector (1 DOWNTO 0);
    MemWrite : OUT std_logic ;
    ALUSrc   : OUT std_logic ;
    RegWrite : OUT std_logic );
END control_unit ;

ARCHITECTURE behavioral OF control_unit IS
BEGIN
    PROCESS ( CU_clock , Instr )
    BEGIN
        IF rising_edge ( CU_clock ) THEN
            CASE Instr IS
                -- add, sub
                WHEN "000000" =>
                    RegDst <= '1 ' ;
                    Branch <= '0 ' ;
                    MemRead <= '0 ' ;
```

DESIGN OF DIGITAL SYSTEMS

```
MemtoReg <= '0 ' ;
ALUOp <= "10 " ;
MemWrite <= '0 ' ;
ALUSrc <= '0 ' ;
RegWrite <= '1 ' ;

-- add
WHEN "001000" =>
    RegDst <= '0 ' ;
Branch <= '0 ' ;
    MemRead <= '0 ' ;
    MemtoReg <= '0 ' ;
    ALUOp <= "00 " ;
    MemWrite <= '0 ' ;
    ALUSrc <= '1 ' ;
    RegWrite <= '1 ' ;

-- lw
WHEN "100011" =>
    RegDst <= '0 ' ;
Branch <= '0 ' ;
    MemRead <= '1 ' ;
    MemtoReg <= '1 ' ;
    ALUOp <= "00 " ;
    MemWrite <= '0 ' ;
    ALUSrc <= '1 ' ;
    RegWrite <= '1 ' ;

-- sw
WHEN "101011" =>
    RegDst <= 'X ' ;
Branch <= '0 ' ;
    MemRead <= '0 ' ;
    MemtoReg <= 'X ' ;
    ALUOp <= "00 " ;
    MemWrite <= '1 ' ;
```

DESIGN OF DIGITAL SYSTEMS

```
        ALUSrc <= '1 ' ;
        RegWrite <= '0 ' ;

-- bne
WHEN "000101" =>
    RegDst <= 'X ' ;
Branch <= '1 ' ;
    MemRead <= '0 ' ;
    MemtoReg <= 'X ' ;
    ALUOp <= "01 " ;
    MemWrite <= '0 ' ;
    ALUSrc <= '0 ' ;
    RegWrite <= '0 ' ;

WHEN others =>
    RegDst <= '0 ' ;
Branch <= '0 ' ;
    MemRead <= '0 ' ;
    MemtoReg <= '0 ' ;
    ALUOp <= "00 " ;
    MemWrite <= '0 ' ;
    ALUSrc <= '0 ' ;
    RegWrite <= '0 ' ;

END CASE?
END IF?
END PROCESS?
END behavioral?
```

control_unit_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY control_unit_tb IS
END control_unit_tb ;
```

DESIGN OF DIGITAL SYSTEMS

ARCHITECTURE testbench OF control_unit_tb IS

COMPONENT control_unit

PORT (

CU_clock : IN std_logic ;

Instr : IN std_logic_vector (5 DOWNTO 0);

RegDst : OUT std_logic ;

Branch : OUT std_logic ;

MemRead : OUT std_logic ;

MemtoReg : OUT std_logic ;

ALUOp : OUT std_logic_vector (1 DOWNTO 0);

MemWrite : OUT std_logic ;

ALUSrc : OUT std_logic ;

RegWrite : OUT std_logic);

END COMPONENT;

SIGNAL CU_clock_tb : std_logic ;

SIGNAL Instr_tb : std_logic_vector (5 DOWNTO 0);

SIGNAL ALUOp_tb : std_logic_vector (1 DOWNTO 0);

SIGNAL RegDst_tb , Branch_tb , MemRead_tb , MemtoReg_tb ,
MemWrite_tb , ALUSrc_tb , RegWrite_tb : std_logic ;

BEGIN

Comp_Connection : control_unit PORT MAP (CU_clock => CU_clock_tb,
Instr => Instr_tb,
RegDst => RegDst_tb,

Branch => Branch_tb ,

MemRead => MemRead_tb,
MemtoReg => MemtoReg_tb,
ALUOp => ALUOp_tb,
MemWrite => MemWrite_tb,
ALUSrc => ALUSrc_tb,

DESIGN OF DIGITAL SYSTEMS

```
RegWrite => RegWrite_tb );
```

```
clock_process : PROCESS
```

```
BEGIN
```

```
    CU_clock_tb <= '0 ';
```

```
wait for 5 ns?
```

```
    CU_clock_tb <= '1 ';
```

```
wait for 5 ns?
```

```
END PROCESS?
```

```
stim_process : PROCESS
```

```
BEGIN
```

```
-- add, sub
```

```
    Instr_tb <= "000000 ";
```

```
wait for 10 ns?
```

```
-- add
```

```
    Instr_tb <= "001000 ";
```

```
wait for 10 ns?
```

```
-- lw
```

```
    Instr_tb <= "100011 ";
```

```
wait for 10 ns?
```

```
-- sw
```

```
    Instr_tb <= "101011 ";
```

```
wait for 10 ns?
```

```
-- bne
```

```
    Instr_tb <= "000101 ";
```

```
wait for 10 ns?
```

```
-- default
```

DESIGN OF DIGITAL SYSTEMS

```
Instr_tb <= "111111 ";  
wait for 10 ns;  
END PROCESS?  
END testbench?
```

6. Unit ALU control

alu_control.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
  
ENTITY alu_control IS  
PORT (  
    ALUOp    : IN std_logic_vector (1 DOWNTO 0);  
    Instr    : IN std_logic_vector (5 DOWNTO 0);  
    ALUCtrl  : OUT std_logic_vector (3 DOWNTO 0));  
END alu_control ;  
  
ARCHITECTURE behavioral OF alu_control IS  
BEGIN  
    PROCESS ( ALUOp , Instr )  
    BEGIN  
        IF ALUOp = "10" THEN -- addi  
            ALUCtrl <= "0001 ";  
        ELSIF ALUOp = "01" THEN  
            ALUCtrl <= "1000"; -- bne  
        ELSIF ALUOp = "00" THEN  
            CASE Instr IS  
            WHEN "100000" => -- add  
                ALUCtrl <= "0100 ";  
            WHEN "100010" => -- sub  
                ALUCtrl <= "0101 ";  
            WHEN others => -- default
```


DESIGN OF DIGITAL SYSTEMS

```
        ALUCtrl <= "1110 ";
END CASE?
ELSE -- default
    ALUCtrl <= "1111 ";
END IF?
END PROCESS?
END behavioral?
```

alu _control_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY alu_control_tb IS
END alu_control_tb ;

ARCHITECTURE testbench OF alu_control_tb IS

    COMPONENT alu_control
    PORT (
        ALUOp    : IN std_logic_vector (1 DOWNTO 0);
        Instr    : IN std_logic_vector (5 DOWNTO 0);
        ALUCtrl  : OUT std_logic_vector (3 DOWNTO 0));
    END COMPONENT;

    SIGNAL ALUOp_ tb : std_logic_vector (1 DOWNTO 0);
    SIGNAL Instr_tb : std_logic_vector (5 DOWNTO 0);
    SIGNAL ALUCtrl_ tb : std_logic_vector (3 DOWNTO 0);

    BEGIN

        Comp_Connection : alu_control PORT MAP ( ALUOp => ALUOp_tb,
                                                    Instr => Instr_tb,
                                                    ALUCtrl => ALUCtrl_tb );
```

DESIGN OF DIGITAL SYSTEMS

```
PROCESS
BEGIN
    -- add
    ALUOp_tb <= "10 ";
    Instr_tb <= "001000 ";
    wait for 10 ns?

    -- bne
    ALUOp_tb <= "01 ";
    Instr_tb <= "000000 ";
    wait for 10 ns?

    -- add
    ALUOp_tb <= "00 ";
    Instr_tb <= "100000 ";
    wait for 10 ns?

    -- sub
    ALUOp_tb <= "00 ";
    Instr_tb <= "100010 ";
    wait for 10 ns?

    -- default
    ALUOp_tb <= "00 ";
    Instr_tb <= "111111 ";
    wait for 10 ns?

    -- default
    ALUOp_tb <= "11 ";
    wait for 10 ns?
END PROCESS?
END testbench?
```

DESIGN OF DIGITAL SYSTEMS

7. PC

program_counter.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY program_counter IS
PORT (
    PC_input : IN std_logic_vector (31 DOWNT0 0);
    PC_clock : IN std_logic ;
    PC_reset : IN std_logic ;
    PC_output : OUT std_logic_vector (31 DOWNT0 0));
END program_counter ;

ARCHITECTURE behavioral OF program_counter IS
BEGIN
    PROCESS( PC_reset , PC_clock )
BEGIN
    IF PC_reset = '1' THEN
        PC_output <= "00000000000000000000000000000000 ";
    END IF?
    IF rising_edge ( PC_clock ) THEN
        PC_output < = PC_input ;
    END IF?
END PROCESS?
END behavioral?
```

program_counter_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY program_counter_tb IS
END program_counter_ tb ;
```

DESIGN OF DIGITAL SYSTEMS

ARCHITECTURE testbench OF program_counter_tb IS

COMPONENT program_counter

PORT (

 PC_input : IN std_logic_vector (31 DOWNT0 0);

 PC_clock : IN std_logic ;

 PC_reset : IN std_logic ;

 PC_output : OUT std_logic_vector (31 DOWNT0 0));

END COMPONENT;

SIGNAL PC_clock_tb , PC_reset_tb : std_logic ;

SIGNAL PC_input_tb , PC_output_tb : std_logic_vector (31 DOWNT0 0);

BEGIN

Comp_Connection : program_counter PORT MAP (PC_input => PC_input_tb,
 PC_clock => PC_clock_tb,
 PC_reset => PC_reset_tb,
 PC_output => PC_output_tb);

clock_process : PROCESS

BEGIN

 PC_clock_tb <= '0 ';

wait for 5 ns?

 PC_clock_tb <= '1 ';

wait for 5 ns?

END PROCESS?

stim_process : PROCESS

BEGIN

 PC_reset_tb <= '1 ';

 PC_input_tb <= "00000000000000000000000000000000 ";

wait for 10 ns?

DESIGN OF DIGITAL SYSTEMS

```
PC_reset_tb <= '0 ' ;

wait for 10 ns?

PC_input_tb <= "00000000000000000000000000000001 " ;

wait for 10 ns?

PC_input_tb <= "00000000000000000000000000000010 " ;

wait for 10 ns?

PC_input_tb <= "00000000000000000000000000000011 " ;

wait for 10 ns?
END PROCESS?
END testbench ;
```

8. 5-fold 2-in-1 multiplexer

mux_5x_2to1.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY mux_5x_2to1 IS
PORT (
Mux5_input1, Mux5_input 2 : IN std_logic_vector (4 DOWNTO 0);
Mux5_S : IN std_logic ;
Mux5_output : OUT std_logic_vector (4 DOWNTO 0));
END mux_5x_ 2to1;

ARCHITECTURE dataflow OF mux_5x_2to1 IS
BEGIN
```

DESIGN OF DIGITAL SYSTEMS

```
Mux5_output <= Mux5_input1 WHEN Mux5_S = '1' ELSE  
Mux5_input2 WHEN Mux5_S = '0 ' ;  
END dataflow;
```

mux_5x_2to1_tb.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
  
ENTITY mux_5x_2to1_tb IS  
END mux_5x_2to1_tb;  
  
ARCHITECTURE testbench OF mux_5x_2to1_tb IS  
  
    COMPONENT mux_5x_2to1  
    PORT (  
        Mux5_input1, Mux5_input 2 : IN std_logic_vector (4 DOWNTO 0);  
        Mux5_S : IN std_logic ;  
        Mux5_output : OUT std_logic_vector (4 DOWNTO 0));  
    END COMPONENT;  
  
    SIGNAL Mux5_input1_tb, Mux5_input2_tb, Mux5_output_tb : std_logic_vector  
        (4 DOWNTO 0);  
    SIGNAL Mux5_S_tb : std_logic ;  
  
    BEGIN  
        Comp_Connection : mux_5x_2to1 PORT MAP (Mux5_input1 => Mux5_input1_tb,  
        Mux5_input2 => Mux5_input2_tb,  
        Mux5_S => Mux5_S_tb,  
        Mux5_output => Mux5_output_tb );  
  
    PROCESS  
    BEGIN  
        Mux5_S_tb <= '0 ' ;  
        wait for 10 ns?
```

DESIGN OF DIGITAL SYSTEMS

```
Mux5_S_tb <= '1 ' ;  
wait for 10 ns?  
END PROCESS?  
  
PROCESS  
BEGIN  
Mux5_input1_tb <= "00000 " ;  
Mux5_input2_tb <= "11111 " ;  
wait for 10 ns?  
END PROCESS?  
END testbench ;
```

16-by-32 character extension unit

sign_extend_16to32.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
  
ENTITY sign_extend_16to32 IS  
PORT (  
    SignExtend_input : IN std_logic_vector (15 DOWNT0 0);  
    SignExtend_output : OUT std_logic_vector (31 DOWNT0 0));  
END sign_extend_16to32;  
  
ARCHITECTURE dataflow OF sign_extend_16to32 IS  
    SIGNAL ones : std_logic_vector (15 DOWNT0 0) := (OTHERS => '1');  
    SIGNAL zeros : std_logic_vector (15 DOWNT0 0) := (OTHERS => '0');  
BEGIN
```

DESIGN OF DIGITAL SYSTEMS

```
        SignExtend_output <= ones & SignExtend_input WHEN SignExtend_input
( 15 ) = '1' ELSE
zeros & SignExtend_input WHEN SignExtend_input ( 15 ) = '0' ;
END dataflow;
```

sign_extend_16to32_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY sign_extend_16to32_tb IS
END sign_extend_16to32_tb;

ARCHITECTURE testbench OF sign_extend_16to32_tb IS

COMPONENT sign_extend_ 16to32
PORT (
        SignExtend_input : IN std_logic_vector (15 DOWNT0 0);
        SignExtend_output : OUT std_logic_vector (31 DOWNT0 0));
END COMPONENT;

SIGNAL SignExtend_input_tb : std_logic_vector (15 DOWNT0 0);
SIGNAL SignExtend_output_tb : std_logic_vector (31 DOWNT0 0);

BEGIN

    Comp_Connection : sign_extend_16to32 PORT MAP ( SignExtend_input =>
SignExtend_input_tb,
                                                    SignExtend_output =>
SignExtend_output_tb );

PROCESS
BEGIN
    SignExtend_input_tb <= "0101010101010101 ";
    wait for 10 ns?
```


DESIGN OF DIGITAL SYSTEMS

```
SignExtend_input_tb <= "1010101010101010 ";  
wait for 10 ns;  
END PROCESS?  
END testbench?
```

10, 11, 12. 32- pl 2- in -1 multiplexer

mux_32x_2to1.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
  
ENTITY mux_32x_2to1 IS  
PORT (  
Mux32_input1, Mux32_input 2 : IN std_logic_vector (31 DOWNT0 0);  
Mux32_S : IN std_logic ;  
Mux32_output : OUT std_logic_vector (31 DOWNT0 0));  
END mux_32x_2to1;  
  
ARCHITECTURE dataflow OF mux_32x_2to1 IS  
BEGIN  
Mux32_output <= Mux32_input1 WHEN Mux32_S = '1' ELSE  
Mux32_input2 WHEN Mux32_S = '0 ';  
END dataflow;
```

mux_32x_2to1_tb.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
  
ENTITY mux_32x_2to1_tb IS  
END mux_32x_2to1_tb;  
  
ARCHITECTURE testbench OF mux_32x_2to1_tb IS
```

DESIGN OF DIGITAL SYSTEMS

```
COMPONENT mux_32x_2to1
PORT (
Mux32_input1, Mux32_input 2 : IN std_logic_vector (31 DOWNT0 0);
Mux32_S : IN std_logic ;
Mux32_output : OUT std_logic_vector (31 DOWNT0 0));
END COMPONENT;

SIGNAL Mux32_input1_tb, Mux32_input2_tb, Mux32_output_tb :
std_logic_vector (31 DOWNT0 0);
SIGNAL Mux32_S_ tb : std_logic ;

BEGIN

    Comp_Connection : mux_32x_2to1 PORT MAP (Mux32_input1 =>
Mux32_input1_tb,
Mux32_input2 => Mux32_input2_tb,
Mux32_S => Mux32_S_tb,
Mux32_output => Mux32_output_tb );

PROCESS

BEGIN
Mux32_S_tb <= '0 ';
wait for 10 ns?
Mux32_S_tb <= '1 ';
wait for 10 ns?
END PROCESS?

PROCESS

BEGIN
Mux32_input1_tb <= "00000000000000000000000000000000 ";
Mux32_input2_tb <= "11111111111111111111111111111111 ";
wait for 10 ns?
END PROCESS?
END testbench ;
```

13. Shift Unit left by 2 (32- bits)

shifter_2left.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all ;

ENTITY shifter_2left IS
PORT (
    shifter_input  : IN std_logic_vector (31 DOWNTO 0);
    shifter_output : OUT std_logic_vector (31 DOWNTO 0));
END shifter_2left;

ARCHITECTURE behavioral OF shifter_2left IS
SIGNAL tmp : unsigned(31 DOWNTO 0);
BEGIN
    tmp <= to_unsigned ( to_integer ( signed( Shifter_input ) ), tmp'length
) SLL 2;

    Shifter_output <= std_logic_vector ( to_signed ( to_integer ( tmp ),
Shifter_output'length ) );
END behavioral;
```

shifter_2left_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY shifter_2left_tb IS
END shifter_2left_tb;

ARCHITECTURE testbench OF shifter_2left_tb IS

COMPONENT shifter_2left
PORT (
    shifter_input  : IN std_logic_vector (31 DOWNTO 0);
```

DESIGN OF DIGITAL SYSTEMS

```
        shifter_output : OUT std_logic_vector (31 DOWNTO 0));  
END COMPONENT;  
  
SIGNAL Shifter_input_tb , Shifter_output_tb : std_logic_vector (31 DOWNTO  
0);  
  
BEGIN  
    Comp_Connection : shifter_2left PORT MAP ( Shifter_input =>  
Shifter_input_tb,  
                                                Shifter_output =>  
Shifter_output_tb );  
PROCESS  
BEGIN  
    Shifter_input_tb <= (others => '0' );  
wait for 10 ns?  
  
    Shifter_input_tb <= (others => '1' );  
wait for 10 ns?  
  
    Shifter_input_tb <= "11001100110011001100110011001100 ";  
wait for 10 ns?  
END PROCESS?  
END testbench?
```

14. Adder 32 bits

pc_adder.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
USE ieee.numeric_std.all ;  
  
ENTITY pc_adder IS  
PORT (  
    previousCmdAddr : IN std_logic_vector (31 DOWNTO 0);
```

DESIGN OF DIGITAL SYSTEMS

```
        nextCmdAddr    : OUT std_logic_vector (31 DOWNTO 0));  
END pc_adder ;  
  
ARCHITECTURE dataflow OF pc_adder IS  
SIGNAL sum : unsigned(31 DOWNTO 0);  
BEGIN  
sum <= unsigned( previousCmdAddr ) + 1;  
    nextCmdAddr <= std_logic_vector (sum );  
END dataflow;
```

pc_adder_tb.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
  
ENTITY pc_adder_tb IS  
END pc_adder_ tb ;  
  
ARCHITECTURE testbench OF pc_adder_tb IS  
  
COMPONENT pc_adder  
PORT (  
    previousCmdAddr : IN std_logic_vector (31 DOWNTO 0);  
    nextCmdAddr     : OUT std_logic_vector (31 DOWNTO 0));  
END COMPONENT;  
  
SIGNAL previousCmdAddr_tb , nextCmdAddr_tb : std_logic_vector (31 DOWNTO 0);  
  
BEGIN  
    Comp_Connection : pc_adder PORT MAP ( previousCmdAddr =>  
previousCmdAddr_tb,  
                                                nextCmdAddr => nextCmdAddr_tb  
);
```

DESIGN OF DIGITAL SYSTEMS

PROCESS

BEGIN

```
previousCmdAddr_tb <= "00000000000000000000000000000000 ";
```

wait for 10 ns?

```
previousCmdAddr_tb <= "00000000000000000000000000000001 ";
```

wait for 10 ns?

```
previousCmdAddr_tb <= "00000000000000000000000000000010 ";
```

wait for 10 ns?

```
previousCmdAddr_tb <= "00000000000000000000000000000011 ";
```

wait for 10 ns?

```
previousCmdAddr_tb <= "11111111111111111111111111111111 ";
```

wait for 10 ns?

```
previousCmdAddr_tb <= "11111111111111111111111111111111 ";
```

wait for 10 ns?

END PROCESS?

END testbench?

15. Adder 32 bits

fullAdder_32bit.vhd

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all;
```

```
USE ieee.std_logic_unsigned.all ;
```

```
USE ieee.numeric_std.all ;
```

```
ENTITY fullAdder_32bit IS
```

```
PORT (
```

```
Adder_input1, Adder_input 2 : IN std_logic_vector (31 DOWNT0 0);
```

DESIGN OF DIGITAL SYSTEMS

```
        Adder_output          : OUT std_logic_vector (31 DOWNTO 0)
    );
END fullAdder_ 32bit;

ARCHITECTURE dataflow OF fullAdder_32bit IS
BEGIN
    Adder_output <= Adder_input1 + Adder_input2 ;
END dataflow;
```

fullAdder_32bit_tb.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY fullAdder_32bit_tb IS
END fullAdder_32bit_ tb;

ARCHITECTURE testbench OF fullAdder_32bit_tb IS

COMPONENT fullAdder_32bit
PORT (
    Adder_input1, Adder_input 2 : IN std_logic_vector (31 DOWNTO 0);
        Adder_Cin                : IN std_logic_vector (0 DOWNTO 0);
        Adder_output              : OUT std_logic_vector (31 DOWNTO 0);
        Adder_Cout                : OUT std_logic );
END COMPONENT;

, Adder_input2_tb, Adder_output_tb : std_logic_vector (31 DOWNTO 0);
SIGNAL Adder_Cin_tb : std_logic_vector (0 DOWNTO 0);
SIGNAL Adder_Cout_ tb : std_logic ;

BEGIN

    Comp_ Connection : fullAdder_32bit PORT MAP (Adder_input1 =>
    Adder_input1_tb,
    Adder_input2 => Adder_input2_tb,
```

DESIGN OF DIGITAL SYSTEMS

```

Adder_Cin => Adder_Cin_tb,
Adder_output =>
Adder_output_tb,

);

PROCESS
BEGIN
Adder_input1_tb <= "010101010101010101010101010101 ";
Adder_input2_tb <= "00110011001100110011001100110011 ";
    Adder_Cin_tb <= "1 ";
wait for 10 ns?

Adder_input1_tb <= "11000011001100110011001100110011 ";
Adder_input2_tb <= "01111111111111111111111111111111 ";
    Adder_Cin_tb <= "0 ";
wait for 10 ns?
END PROCESS?
END testbench?
```

input AND gate

and2_gate.vhd

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY and_2gate IS
PORT (
Branch, Zero : IN std_logic ;
    AND_output  : OUT std_logic );
END and_2gate;

ARCHITECTURE dataflow OF and_2gate IS
BEGIN
```


DESIGN OF DIGITAL SYSTEMS

```
    AND_output <= Branch AND Zero;  
END dataflow;
```

and2_gate_tb.vhd

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
  
ENTITY and_2gate_tb IS  
END and_2gate_tb;  
  
ARCHITECTURE testbench OF and_2gate_tb IS  
  
    COMPONENT and_2gate  
    PORT (  
        Branch, Zero : IN std_logic ;  
            AND_output      : OUT std_logic );  
    END COMPONENT;  
  
    SIGNAL Branch_tb , Zero_tb , AND_output_tb : std_logic ;  
  
    BEGIN  
        Comp_Connection : and_2gate PORT MAP (Branch => Branch_tb ,  
        Zero => Zero_tb ,  
                                                    AND_output => AND_output_tb );  
  
    PROCESS  
    BEGIN  
        Branch_tb <= '0'; Zero_tb <= '0 '  
wait for 10 ns?  
        Branch_tb <= '1'; Zero_tb <= '0 ';
```

DESIGN OF DIGITAL SYSTEMS

```
wait for 10 ns?
    Branch_tb <= '0'; Zero_tb <= '1 ';
wait for 10 ns?
    Branch_tb <= '1'; Zero_tb <= '1 ';
wait for 10 ns?
END PROCESS?
END testbench?
```

MIPS

19390005_ATHANASIOU_02_MIPS.vhd

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_signed.all ;

ENTITY MIPS IS
PORT (
    MIPS_ clock : IN std_logic ;
    MIPS_ reset : IN std_logic ;
    PC_output_ MIPS : OUT std_logic_vector (31 DOWNT0 0);
    ALU_output_ MIPS : OUT std_logic_vector (31 DOWNT0 0);
    zeroSig_MIPS  : OUT std_logic ;
    readData1_ MIPS : OUT std_logic_vector (31 DOWNT0 0);
    readData2_ MIPS : OUT std_logic_vector (31 DOWNT0 0);
    Branch_MIPS   : OUT std_logic ;
    instrOut_ MIPS : OUT std_logic_vector (31 DOWNT0 0);
    writeData_ MIPS : OUT std_logic_vector (31 DOWNT0 0);
    MemWrite_ MIPS : OUT std_logic ;
    RegWrite_ MIPS : OUT std_logic
);
END MIPS?

ARCHITECTURE structural OF MIPS IS
```

DESIGN OF DIGITAL SYSTEMS

```
COMPONENT alu
PORT (
    operationSig : IN std_logic_vector (3 DOWNTO 0);
    ALU_input1   : IN std_logic_vector (31 DOWNTO 0);
    ALU_input2   : IN std_logic_vector (31 DOWNTO 0);
    ALU_output    : OUT std_logic_vector (31 DOWNTO 0);
    zeroSig      : OUT std_logic );
END COMPONENT;
```

```
COMPONENT register_file
PORT (
    RF_clock      : IN std_logic ;
    RF_reset      : IN std_logic ;
    readReg1      : IN std_logic_vector (4 DOWNTO 0);
    readReg2      : IN std_logic_vector (4 DOWNTO 0);
    writeRegIn    : IN std_logic_vector (4 DOWNTO 0);
    writeData     : IN std_logic_vector (31 DOWNTO 0);
    RegWrite      : IN std_logic ;
    readData1     : OUT std_logic_vector (31 DOWNTO 0);
    readData2     : OUT std_logic_vector (31 DOWNTO 0));
END COMPONENT;
```

```
COMPONENT data_memory
PORT (
    writeData     : IN std_logic_vector (31 DOWNTO 0);
    addr          : IN std_logic_vector (31 DOWNTO 0);
    MemRead       : IN std_logic ;
    MemWrite      : IN std_logic ;
    readData      : OUT std_logic_vector (31 DOWNTO 0));
END COMPONENT;
```

```
COMPONENT instructions_memory
```

DESIGN OF DIGITAL SYSTEMS

```
PORT (  
    readAddr  : IN std_logic_vector (31 DOWNTO 0);  
    instrOut   : OUT std_logic_vector (31 DOWNTO 0));  
END COMPONENT;
```

```
COMPONENT control_unit
```

```
PORT (  
    CU_clock : IN std_logic ;  
    Instr    : IN std_logic_vector (5 DOWNTO 0);  
    RegDst   : OUT std_logic ;  
Branch : OUT std_logic ;  
    MemRead  : OUT std_logic ;  
    MemtoReg : OUT std_logic ;  
    ALUOp    : OUT std_logic_vector (1 DOWNTO 0);  
    MemWrite : OUT std_logic ;  
    ALUSrc   : OUT std_logic ;  
    RegWrite : OUT std_logic );  
END COMPONENT;
```

```
COMPONENT alu_control
```

```
PORT (  
    ALUOp    : IN std_logic_vector (1 DOWNTO 0);  
    Instr    : IN std_logic_vector (5 DOWNTO 0);  
    ALUCtrl  : OUT std_logic_vector (3 DOWNTO 0));  
END COMPONENT;
```

```
COMPONENT program_counter
```

```
PORT (  
    PC_input : IN std_logic_vector (31 DOWNTO 0);  
    PC_clock : IN std_logic ;  
    PC_reset : IN std_logic ;  
    PC_output : OUT std_logic_vector (31 DOWNTO 0));  
END COMPONENT;
```

DESIGN OF DIGITAL SYSTEMS

```
COMPONENT pc_adder
```

```
PORT (
```

```
    previousCmdAddr : IN std_logic_vector (31 DOWNTO 0);
```

```
    nextCmdAddr      : OUT std_logic_vector (31 DOWNTO 0));
```

```
END COMPONENT;
```

```
COMPONENT mux_5x_2to1
```

```
PORT (
```

```
Mux5_input1, Mux5_input 2 : IN std_logic_vector (4 DOWNTO 0);
```

```
Mux5_S : IN std_logic ;
```

```
Mux5_output : OUT std_logic_vector (4 DOWNTO 0));
```

```
END COMPONENT;
```

```
COMPONENT sign_extend_16to32
```

```
PORT (
```

```
    SignExtend_input : IN std_logic_vector (15 DOWNTO 0);
```

```
    SignExtend_output : OUT std_logic_vector (31 DOWNTO 0));
```

```
END COMPONENT;
```

```
COMPONENT mux_32x_2to1
```

```
PORT (
```

```
Mux32_input1, Mux32_input 2 : IN std_logic_vector (31 DOWNTO 0);
```

```
Mux32_S : IN std_logic ;
```

```
Mux32_output : OUT std_logic_vector (31 DOWNTO 0));
```

```
END COMPONENT;
```

```
COMPONENT shifter_2left
```

```
PORT (
```

```
    shifter_input : IN std_logic_vector (31 DOWNTO 0);
```

```
    shifter_output : OUT std_logic_vector (31 DOWNTO 0));
```

```
END COMPONENT;
```

```
COMPONENT fullAdder_32bit
```

DESIGN OF DIGITAL SYSTEMS

```
PORT (  
Adder_input1, Adder_input 2 : IN std_logic_vector (31 DOWNT0 0);  
    Adder_output              : OUT std_logic_vector (31 DOWNT0 0));  
END COMPONENT;  
  
COMPONENT and_2gate  
PORT (  
Branch, Zero : IN std_logic ;  
    AND_output      : OUT std_logic );  
END COMPONENT;  
  
-- ALU out signals  
SIGNAL ALU_output_ Sig : std_logic_vector (31 DOWNT0 0);  
SIGNAL zeroSig_Sig   : std_logic ;  
  
-- Register File out signals  
SIGNAL readData1_ Sig : std_logic_vector (31 DOWNT0 0);  
SIGNAL readData2_ Sig : std_logic_vector (31 DOWNT0 0);  
SIGNAL writeData_ Sig : std_logic_vector (31 DOWNT0 0);  
  
-- Data Memory out signals  
SIGNAL readDataMemory_ Sig : std_logic_vector (31 DOWNT0 0);  
  
-- Instructions Memory out signals  
SIGNAL instrOut_ Sig : std_logic_vector (31 DOWNT0 0);  
  
-- Control Unit  
SIGNAL Instr_Sig      : std_logic_vector (5 DOWNT0 0);  
SIGNAL RegDst_Sig     : std_logic ;  
SIGNAL Branch_Sig     : std_logic ;  
SIGNAL MemRead_Sig    : std_logic ;  
SIGNAL MemtoReg_ Sig  : std_logic ;  
SIGNAL ALUOp_Sig      : std_logic_vector (1 DOWNT0 0);  
SIGNAL MemWrite_ Sig  : std_logic ;
```

DESIGN OF DIGITAL SYSTEMS

```
SIGNAL ALUSrc_Sig : std_logic ;
SIGNAL RegWrite_ Sig : std_logic ;

-- ALU Control out signals
SIGNAL ALUCtrl_ Sig : std_logic_vector (3 DOWNT0 0);

-- Program Counter out signals
SIGNAL PC_output_ Sig : std_logic_vector (31 DOWNT0 0);

-- PC Adder out signals
SIGNAL nextCmdAddr_ Sig : std_logic_vector (31 DOWNT0 0);

-- Mux 5x 2-to-1 out signals
SIGNAL Mux5_output_ Register : std_logic_vector (4 DOWNT0 0);

-- Sign Extend 16-to-32 out signals
SIGNAL SignExtend_output_ Sig : std_logic_vector (31 DOWNT0 0);

-- Mux 32x 2-to-1 out signals
SIGNAL Mux32_output_PC : std_logic_vector (31 DOWNT0 0);
SIGNAL Mux32_output_ALU : std_logic_vector (31 DOWNT0 0);
SIGNAL Mux32_output_ Register : std_logic_vector (31 DOWNT0 0);

-- Shifter 2 Left out signals
SIGNAL Shifter_output_ Sig : std_logic_vector (31 DOWNT0 0);

-- Full Adder 32- bit out signals
SIGNAL Adder_output_ Sig : std_logic_vector (31 DOWNT0 0);
SIGNAL Adder_Cout_Sig : std_logic ;

-- AND 2-gate out signals
SIGNAL AND_output_ Sig : std_logic ;
```

DESIGN OF DIGITAL SYSTEMS

BEGIN

```
PC_output_MIPS    <= PC_output_ Sig ;
instrOut_MIPS     <= instrOut_ Sig ;
ALU_output_MIPS   <= ALU_output_ Sig ;
readData1_MIPS    <= readData1_ Sig;
readData2_MIPS    <= readData2_ Sig;
writeData_MIPS     <= readDataMemory_Sig WHEN MemtoReg_Sig = '1' ELSE
ALU_output_Sig ;
Branch_MIPS        < = Branch_Sig ;
zeroSig_MIPS       <= zeroSig_ Sig ;
RegWrite_MIPS     <= RegWrite_ Sig ;
MemWrite_MIPS     <= MemWrite_ Sig ;

PCAdder : pc_adder PORT MAP ( previousCmdAddr => PC_output_Sig ,
                             nextCmdAddr => nextCmdAddr_Sig );

BranchAdder : fullAdder_32bit PORT MAP (Adder_input1 => nextCmdAddr_Sig ,
Adder_input2 => Shifter_output_Sig ,
                                     Adder_output => Adder_output_Sig
);

ProgramCounter : program_counter PORT MAP ( PC_input => Mux32_output_PC,
                                           PC_clock => MIPS_clock,
                                           PC_reset => MIPS_reset,
                                           PC_output => PC_output_Sig );

InstructionsMemory : instructions_memory PORT MAP ( readAddr =>
PC_output_Sig,
                                           instrOut =>
instrOut_Sig );

RegisterFile : register_file PORT MAP ( RF_clock => MIPS_clock,
                                       RF_reset => MIPS_reset,
readReg1 => instrOut_ Sig ( 25 DOWNT0 21),
```


DESIGN OF DIGITAL SYSTEMS

```
readReg2 => instrOut_ Sig ( 20 DOWNT0 16),
                                                    writeRegIn =>
Mux5_output_Register,
                                                    writeData =>
Mux32_output_Register,
                                                    RegWrite => RegWrite_Sig,

readData1 => readData1_Sig,
readData2 => readData2_Sig );

Control Unit : control_unit PORT MAP ( CU_clock => MIPS_clock,
                                                    Instr => instrOut_ Sig ( 31 DOWNT0
26),
                                                    RegDst => RegDst_Sig,

Branch => Branch_Sig ,
                                                    MemRead => MemRead_Sig,
                                                    MemtoReg => MemtoReg_Sig,
                                                    ALUOp => ALUOp_Sig,
                                                    MemWrite => MemWrite_Sig,
                                                    ALUSrc => ALUSrc_Sig,
                                                    RegWrite => RegWrite_Sig );

ALUControl : alu_control PORT MAP ( ALUOp => ALUOp_Sig,
                                                    Instr => instrOut_ Sig ( 5 DOWNT0 0 ),
ALUCtrl => ALUCtrl_Sig );

ArithmeticLogicUnit : alu PORT MAP ( operationSig => ALUCtrl_Sig,
ALU_input1 => readData1_Sig,
ALU_input2 => Mux32_output_ALU,
                                                    ALU_output => ALU_output_Sig,
                                                    zeroSig => zeroSig_Sig );

DataMemory : data_memory PORT MAP ( writeData => readData2_Sig,
                                                    addr => ALU_output_Sig,
                                                    MemRead => MemRead_Sig,
```

DESIGN OF DIGITAL SYSTEMS

```
MemWrite => MemWrite_Sig,  
readData => readDataMemory_Sig );
```

```
Mux5x2to1_ Register : mux_5x_2to1 PORT MAP (Mux5_input1 => instrOut_Sig  
(20 DOWNTO 16),
```

```
Mux5_input2 => instrOut_Sig ( 15 DOWNTO 11),
```

```
Mux5_S => RegDst_Sig ,
```

```
Mux5_output => Mux5_output_Register );
```

```
Mux32x2to1_ ALU : mux_32x_2to1 PORT MAP (Mux32_input1 => readData2_Sig,
```

```
Mux32_input2 => SignExtend_output_Sig ,
```

```
Mux32_S => ALUSrc_Sig ,
```

```
Mux32_output => Mux32_output_ALU );
```

```
Mux32x2to1_ Register : mux_32x_2to1 PORT MAP (Mux32_input1 =>  
readDataMemory_Sig ,
```

```
Mux32_input2 => ALU_output_Sig ,
```

```
Mux32_S => MemtoReg_Sig ,
```

```
Mux32_output => Mux32_output_Register );
```

```
Mux32x2to1_ PC : mux_32x_2to1 PORT MAP (Mux32_input1 => nextCmdAddr_Sig ,
```

```
Mux32_input2 => Adder_output_Sig ,
```

```
Mux32_S => AND_output_Sig ,
```

```
Mux32_output => Mux32_output_PC );
```

```
SignExtend16to 32 : sign_extend_16to32 PORT MAP ( SignExtend_input =>  
instrOut_Sig (15 DOWNTO 0),
```

```
SignExtend_output =>  
SignExtend_output_Sig );
```

```
AND2 gate : and_2gate PORT MAP (Branch => Branch_Sig ,
```

```
Zero => zeroSig_Sig ,
```

```
AND_output => AND_output_Sig );
```

DESIGN OF DIGITAL SYSTEMS

```
Shifter2 Left : shifter_2left PORT MAP ( Shifter_input =>
SignExtend_output_Sig,

Shifter_output =>
Shifter_output_Sig );
```

```
END structural;
```

19390005_ATHANASIOU_03_testbench.vhd

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY MIPS_tb IS
```

```
END MIPS_ tb ;
```

```
ARCHITECTURE testbench OF MIPS_tb IS
```

```
MIPS COMPONENTS
```

```
PORT (
```

```
    MIPS_ clock : IN std_logic ;
```

```
    MIPS_ reset : IN std_logic ;
```

```
    PC_output_ MIPS : OUT std_logic_vector (31 DOWNTO 0);
```

```
    ALU_output_ MIPS : OUT std_logic_vector (31 DOWNTO 0);
```

```
    zeroSig_MIPS   : OUT std_logic ;
```

```
readData1_ MIPS : OUT std_logic_vector (31 DOWNTO 0);
```

```
readData2_ MIPS : OUT std_logic_vector (31 DOWNTO 0);
```

```
    Branch_MIPS   : OUT std_logic ;
```

```
    instrOut_ MIPS : OUT std_logic_vector (31 DOWNTO 0);
```

```
    writeData_ MIPS : OUT std_logic_vector (31 DOWNTO 0);
```

```
    MemWrite_ MIPS : OUT std_logic ;
```

```
    RegWrite_ MIPS : OUT std_logic
```

```
);
```

```
END COMPONENT;
```

```
SIGNAL MIPS_clock_tb      : std_logic := '0';
```

```
SIGNAL MIPS_reset_tb      : std_logic := '0';
```

DESIGN OF DIGITAL SYSTEMS

```
SIGNAL PC_output_tb          : std_logic_vector (31 DOWNT0 0) := (others =>
'0');

SIGNAL ALU_output_tb         : std_logic_vector (31 DOWNT0 0) := (others =>
'0');

SIGNAL zeroSig_tb           : std_logic := '0';

SIGNAL readData1_tb : std_logic_vector (31 DOWNT0 0) := (others => '0');
SIGNAL readData2_tb : std_logic_vector (31 DOWNT0 0) := (others => '0');
SIGNAL Branch_tb         : std_logic := '0';

SIGNAL instrOut_ tb : std_logic_vector (31 DOWNT0 0) := (others => '0');
SIGNAL writeData_tb      : std_logic_vector (31 DOWNT0 0) := (others =>
'0');

SIGNAL MemWrite_tb       : std_logic := '0';
SIGNAL RegWrite_tb       : std_logic := '0';

BEGIN

MIPS_testbench : MIPS PORT MAP (
    MIPS_clock => MIPS_clock_tb ,
    MIPS_reset => MIPS_reset_tb ,
    PC_output_MIPS => PC_output_tb ,
    ALU_output_MIPS => ALU_output_tb ,
    zeroSig_MIPS => zeroSig_tb ,
readData1_MIPS => readData1_tb,
readData2_MIPS => readData2_tb,
    Branch_MIPS => Branch_tb ,
    instrOut_MIPS => instrOut_tb ,
    writeData_MIPS => writeData_tb ,
    MemWrite_MIPS => MemWrite_tb ,
    RegWrite_MIPS => RegWrite_tb
);

clock_process : PROCESS
BEGIN
    MIPS_clock_tb <= '0 ' ;
wait for 5 ns?
```

DESIGN OF DIGITAL SYSTEMS

```
MIPS_clock_tb <= '1 ';
```

wait for 5 ns?

END PROCESS?


```
reset_process : PROCESS
```

BEGIN

```
    MIPS_reset_tb <= '1 ';
```

wait for 10 ns?

```
    MIPS_reset_tb <= '0 ';
```

wait?


END PROCESS?

END testbench?


DESIGN OF DIGITAL SYSTEMS

3. Screenshot from her implementation

Before execution

 


1 ° clock

 


DESIGN OF DIGITAL SYSTEMS


2 ° clock

 

3 ° clock

 


4 ° clock

 


DESIGN OF DIGITAL SYSTEMS


5 ° clock

 

6 ° clock

 

7 ° clock

 

DESIGN OF DIGITAL SYSTEMS



Thank you for your attention.

